

Story so far

- simplest description of computer?
- what makes it general purpose?

CPU



Memory




Story so far

- simplest description of computer?
- what makes it general purpose?

CPU


Memory

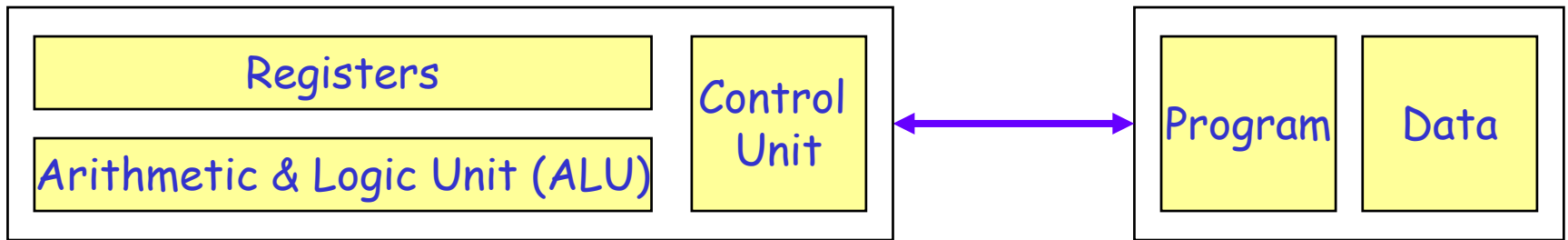

- this lecture: internal structure of the CPU
 - how it relates to the instruction set

CPU organisation: overview

CPU

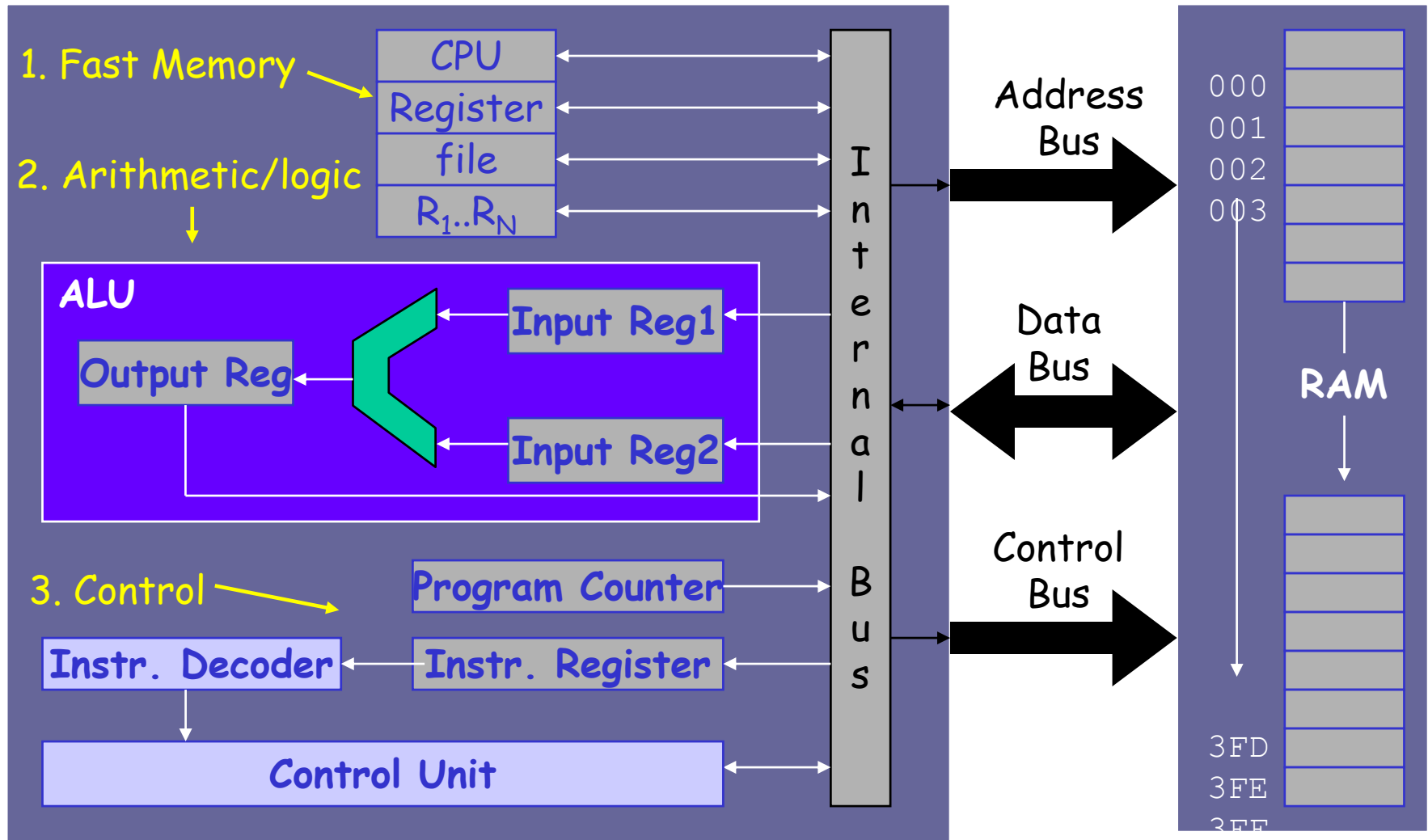

TOY1 instruction set

OPCODE REG ADDRESS

4-bit	2-bit	10-bit
-------	-------	--------

Opcode	Assembly Instruction		Action	
0000	STOP		Stop Program Execution	if opcode=LOAD then Rn = (a) if opcode=ADD then Rn = (b)
0001	LOAD	Rn, [Addr]	Rn = Memory [Addr]	(a)
0010	STORE	Rn, [Addr]	Memory [Addr] = Rn	
0011	ADD	Rn, [Addr]	Rn = Rn + Memory [Addr]	(b)
0100	SUB	Rn, [Addr]	Rn = Rn - Memory [Addr]	
0101	GOTO	Addr	PC = Addr	
0110	IFZER	Rn, Addr	IF Rn == 0 THEN PC = Addr	
0111	IFNEG	Rn, Addr	IF Rn < 0 THEN PC = Addr	

Micro-steps: LOAD R2,[201H]

Control Unit Action FETCH INSTRUCTION¹²

PC to Address Bus ¹³	080H	→	080H	Address Bus
0 to Control Bus ¹⁴	0	→	0	Control Bus
Address Bus to Memory	080H	→	080H	Memory
Control Bus to Memory	0	READ	0	Memory
Increment PC ¹⁵	080	INC	081H	PC becomes PC+1 ¹⁶
Memory [080H] to Data Bus	1A01H	→	1A01H	Data Bus
Data Bus to Instruction Register	1A01H	→	1A01H	Instruction Register

DECODE INSTRUCTION

IR to Instruction Decoder	1A01H	→	1A01H	Instruction Decoder
Instruction Decoder to Control Unit ¹⁷	1, 2, 201H	→	1, 2, 201H	Control Unit

EXECUTE INSTRUCTION¹⁸


Control Unit to Address Bus	201H	→	201H	Address Bus
0 to Control Bus	0	→	0	Control Bus
Address Bus to Memory	201H	→	201H	Memory
Control Bus to Memory	0	READ	0	Memory
Memory [201H] to Data bus	0009H	→	0009H	Data Bus
Data Bus to Register 2	0009H	→	0009H	Register 2

Understand CPU structure

- step by step
 - step 1: just main elements, no connections, no control
 - step 2: add control elements, e.g. multiplexers (mux)
 - step 3: derive control signals: next lecture
- Register Transfer Level (RTL) description: simple
 - 6 registers: PC, IR, A_1 , A_2 , A_{out} , MDR (memory data register)
 - 2 components respond in same cycle: UX, ALU, combinational
 - 2 components have Read and Write signals: Memory, Register file
- circuit diagram (see notes on *basic logic design*)
 - with or without control elements (e.g. mux)
 - with or without control unit


Abstraction: include the minimum

Control and next
instruction logic

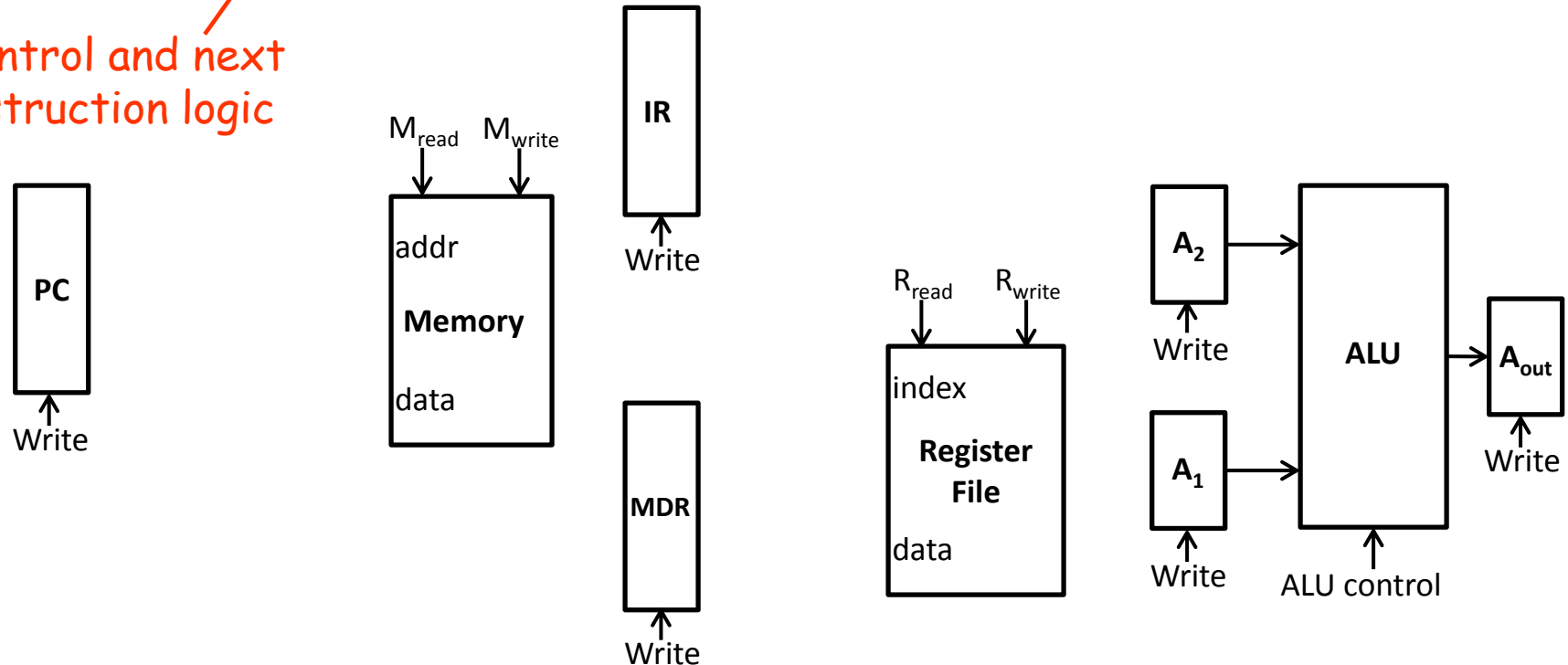


if ALU Control = 0 then $A_{out} = A_1 + A_2$
if ALU Control = 1 then $A_{out} = A_1 - A_2$

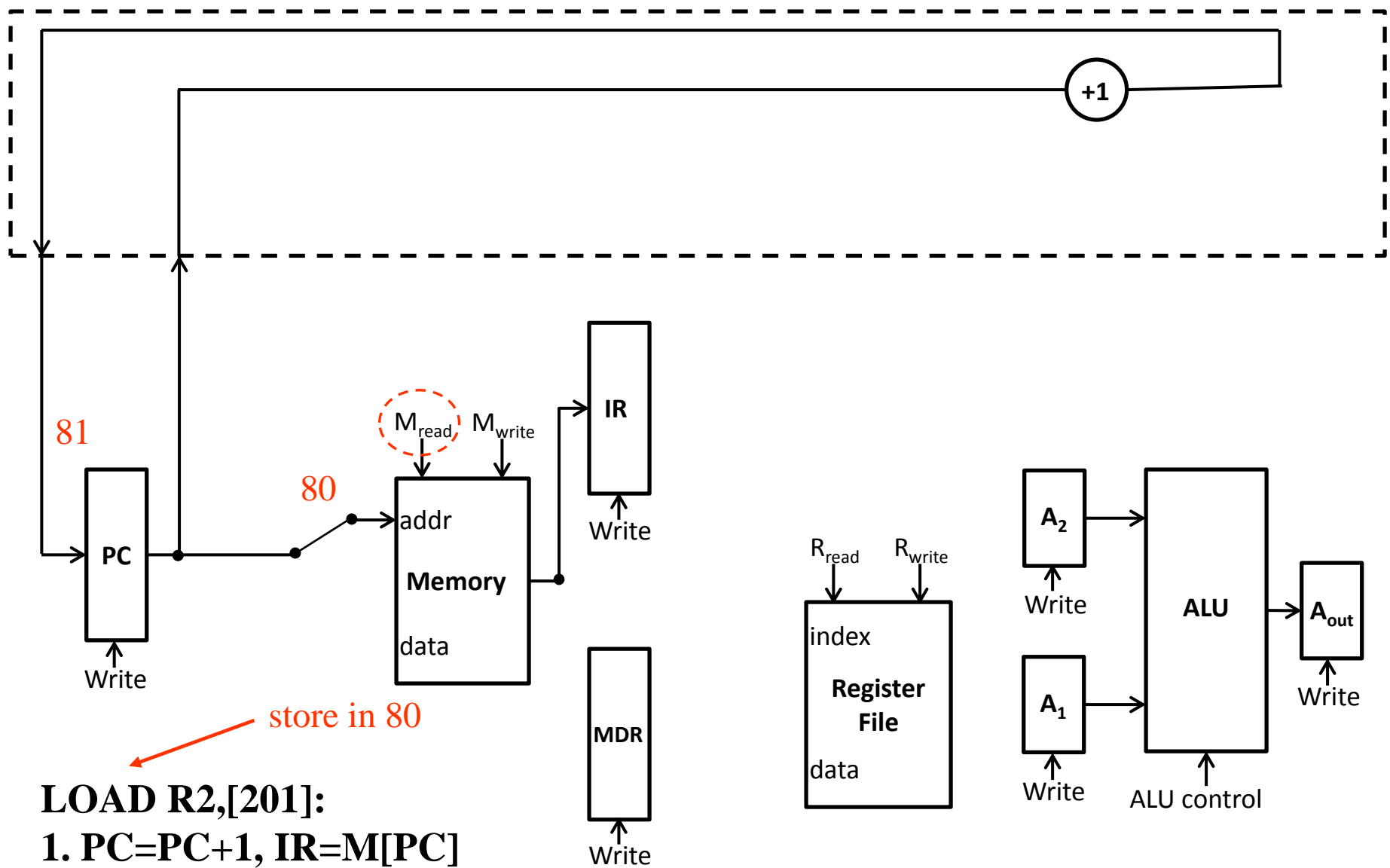10 read/write signals
1 ALU Control signal



if ALU Control = 0 then $A_{out} = A_1 + A_2$
 if ALU Control = 1 then $A_{out} = A_1 - A_2$

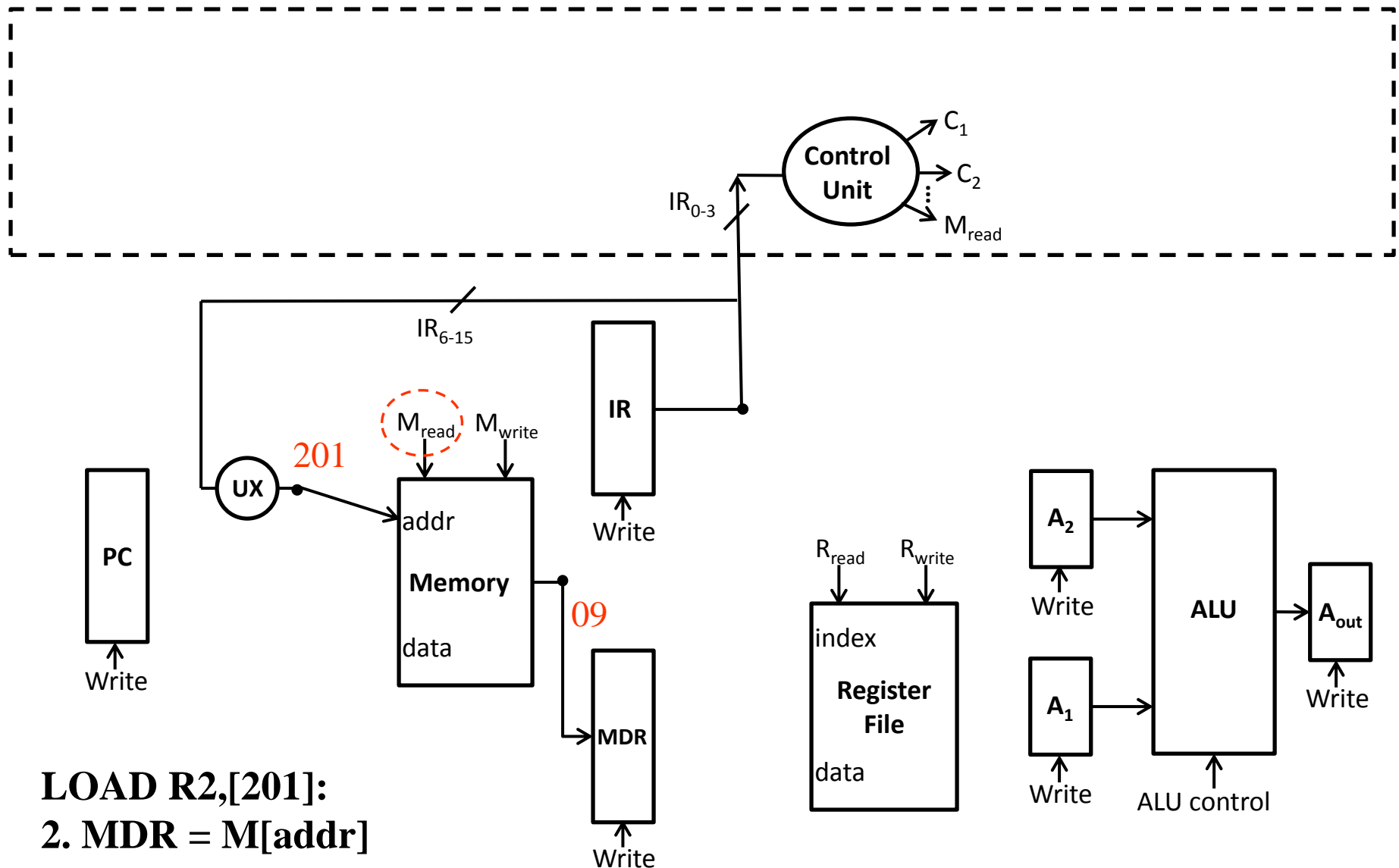10 read/write signals
 1 ALU Control signal




LOAD R2,[201]:
2. MDR = M[addr]
addr = UX(IR_{6..15})


UX: Unsign eXtension
from 10 to 16 bits

if ALU Control = 0 then $A_{out} = A_1 + A_2$
 if ALU Control = 1 then $A_{out} = A_1 - A_2$

 10 read/write signals
 1 ALU Control signal




LOAD R2,[201]:
3. $R[IR_{4..5}] = MDR$

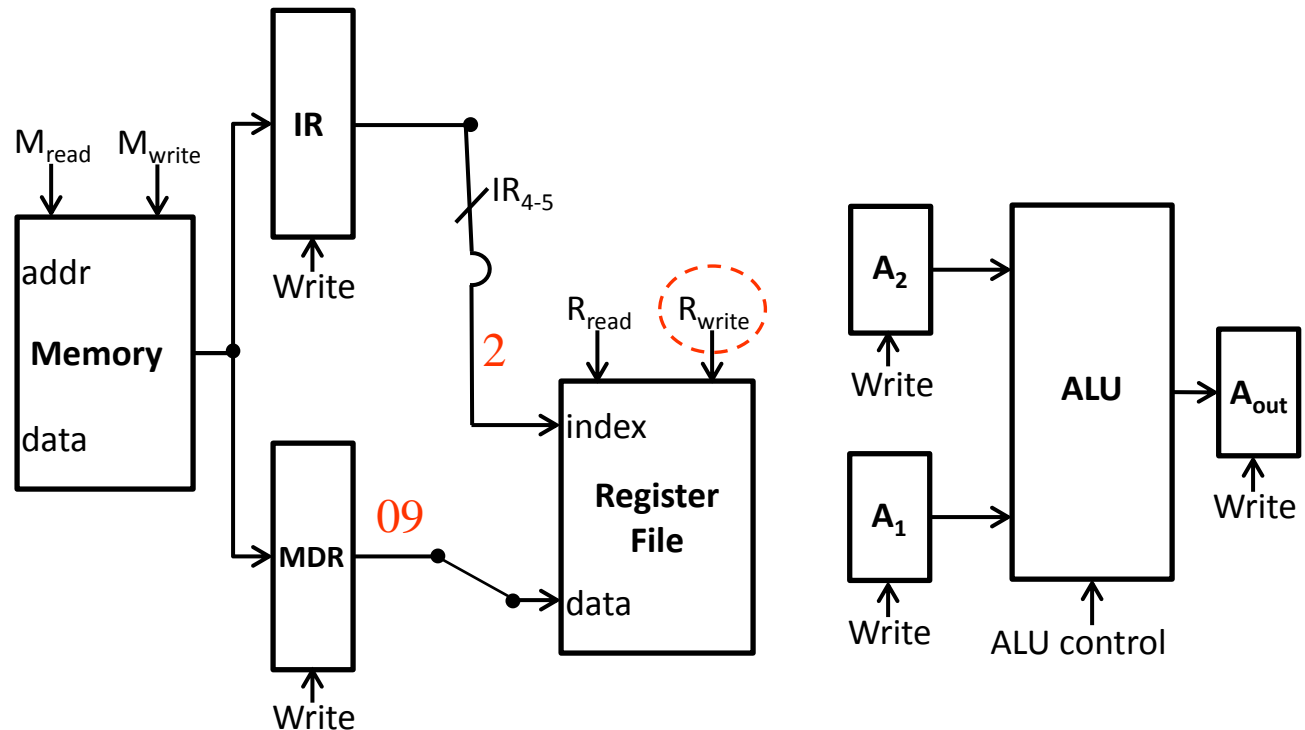

if ALU Control = 0 then $A_{out} = A_1 + A_2$
 if ALU Control = 1 then $A_{out} = A_1 - A_2$

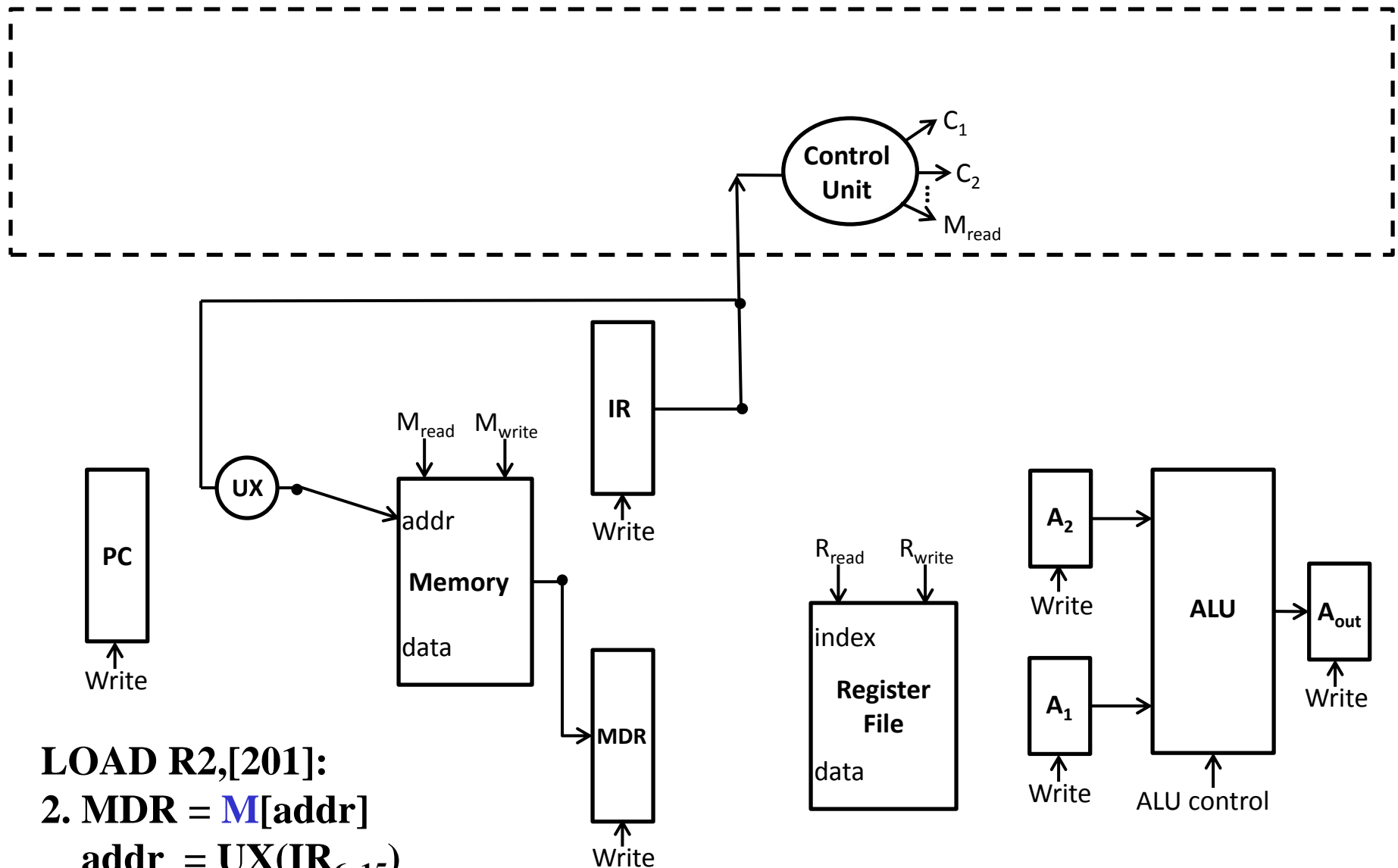
10 read/write signals
 1 ALU Control signal




LOAD R2,[201]:
2. $MDR = M[addr]$
 $addr = UX(IR_{6..15})$

but step 1: $IR = M[PC]$ if ALU Control = 0 then $A_{out} = A_1 + A_2$
so need mux if ALU Control = 1 then $A_{out} = A_1 - A_2$

 10 read/write signals
 1 ALU Control signal



include mux M_1

 

if ALU Control = 0 then $A_{out} = A_1 + A_2$
 if ALU Control = 1 then $A_{out} = A_1 - A_2$

10 read/write signals
 1 ALU Control signal
 1 multiplexer signal

Micro-steps: ADD R2,[202]

Control Unit Action FETCH INSTRUCTION


PC to Address Bus	081H	————→	081H	Address Bus
0 to Control Bus	0	————→	0	Control Bus
Address Bus to Memory	081H	————→	081H	Memory
Control Bus to Memory	0	READ ————→	0	Memory
Increment PC	081H	INC ————→	082H	PC becomes PC+1
Memory [081H] to Data Bus	3A02H	————→	3A02H	Data Bus
Data Bus to Instruction Register	3A02H	————→	3A02H	Instruction Register

DECODE INSTRUCTION

IR to Instruction Decoder	3A02H	————→	3A02H	Instruction Decoder
Instruction Decoder to Control Unit	3, 2, 202H	————→	3, 2, 202H	Control Unit


EXECUTE INSTRUCTION

Register 2 to ALU Input Reg 1	0009	————→	0009	ALU Input Reg 1
Control Unit to Address Bus	202H	————→	202H	Address Bus
0 to Control Bus	0	————→	0	Control Bus
Address Bus to Memory	202H	————→	202H	Memory
Control Bus to Memory	0	READ ————→	0	Memory
Memory [202H] to Data bus	0006H	————→	0006H	Data Bus
Data Bus to ALU Input Reg 2	0006H	————→	0006H	ALU Input Reg 2
Control Unit to ALU		ADD ————→	000FH	Output Register
ALU Output Reg to Register 2	000F	————→	000FH	Register 2

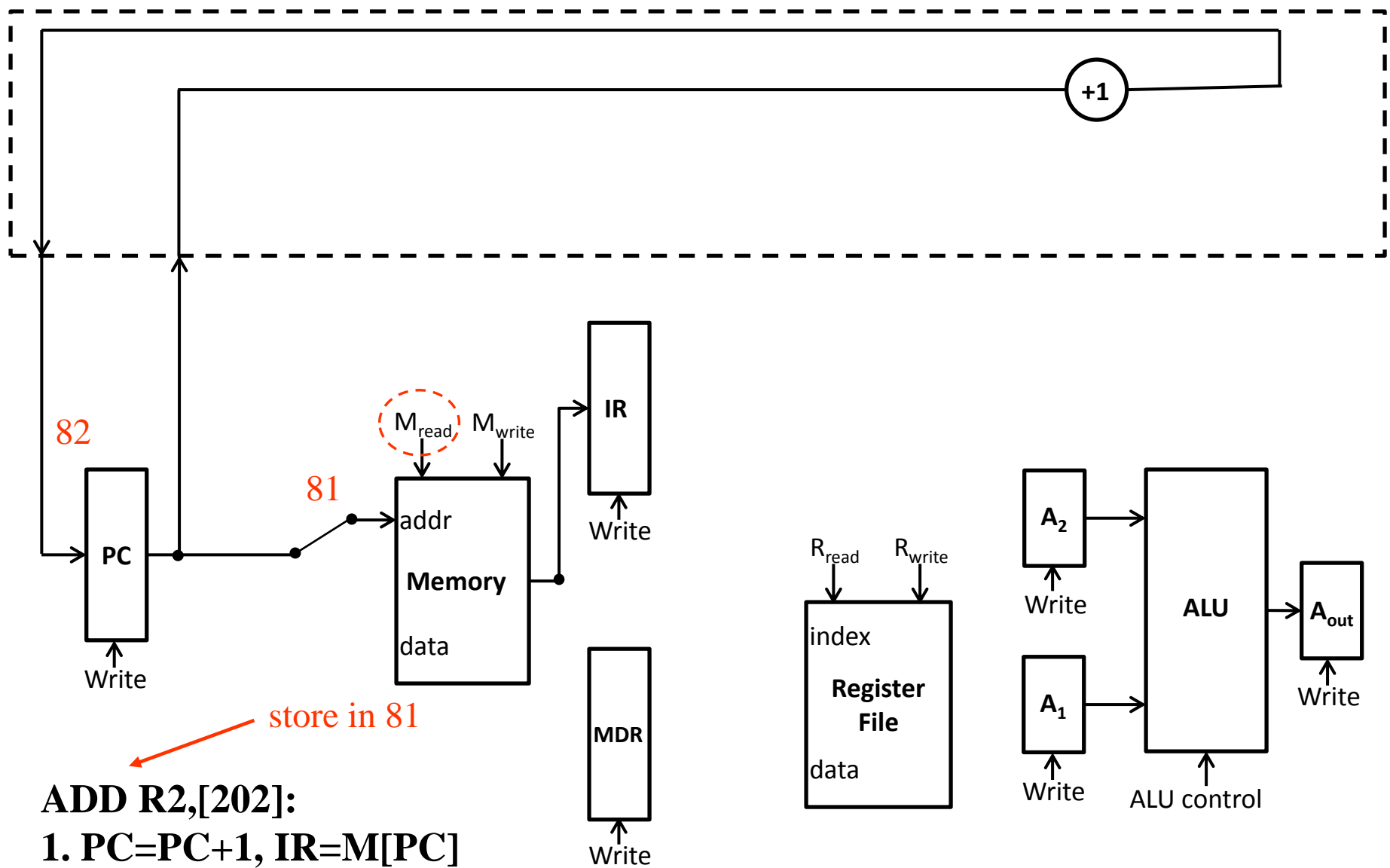

if ALU Control = 0 then $A_{out} = A_1 + A_2$
 if ALU Control = 1 then $A_{out} = A_1 - A_2$

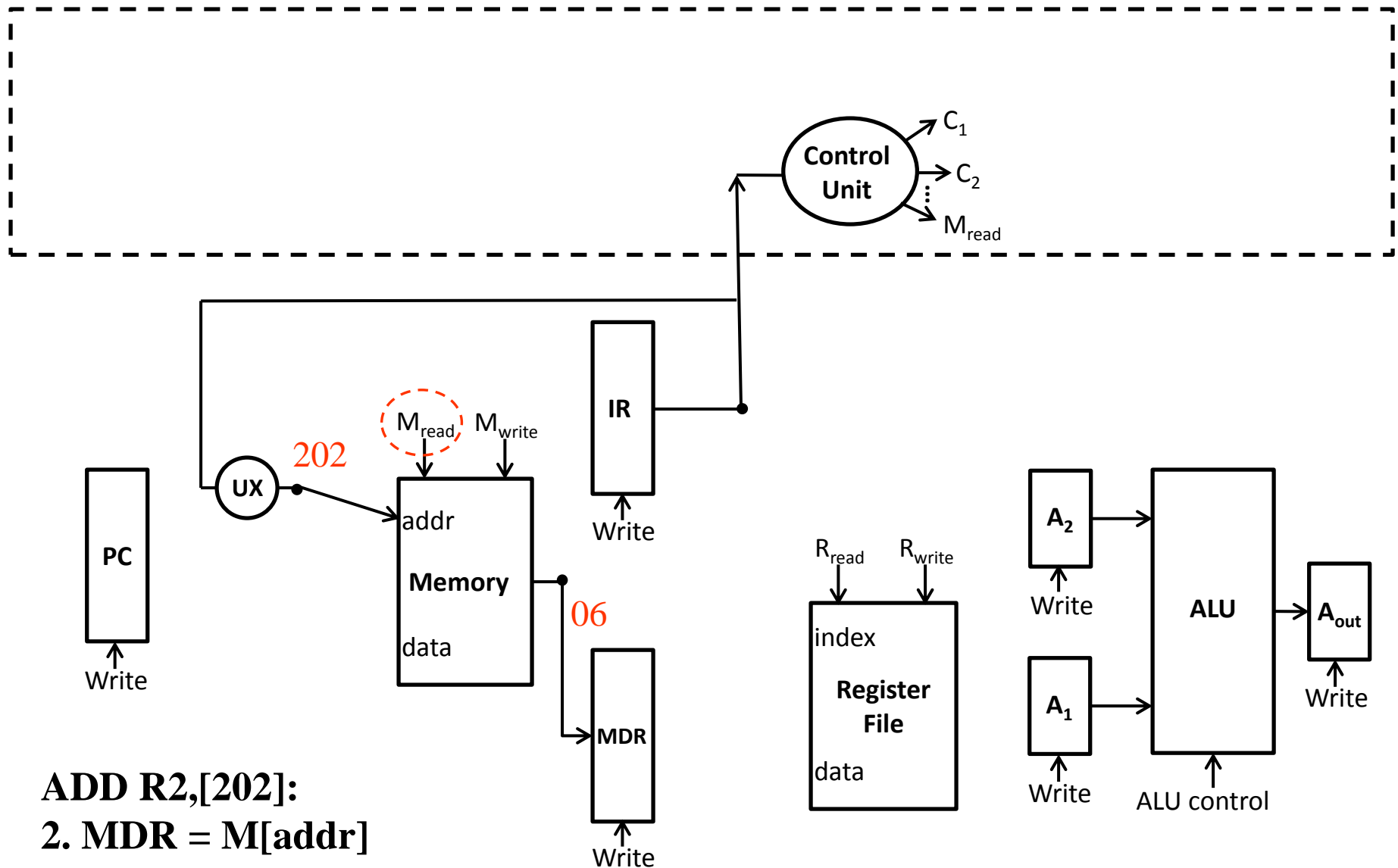10 read/write signals
 1 ALU Control signal




ADD R2,[202]:
2. MDR = M[addr]
addr = UX(IR_{6..15})

if ALU Control = 0 then $A_{out} = A_1 + A_2$
 if ALU Control = 1 then $A_{out} = A_1 - A_2$




10 read/write signals
 1 ALU Control signal

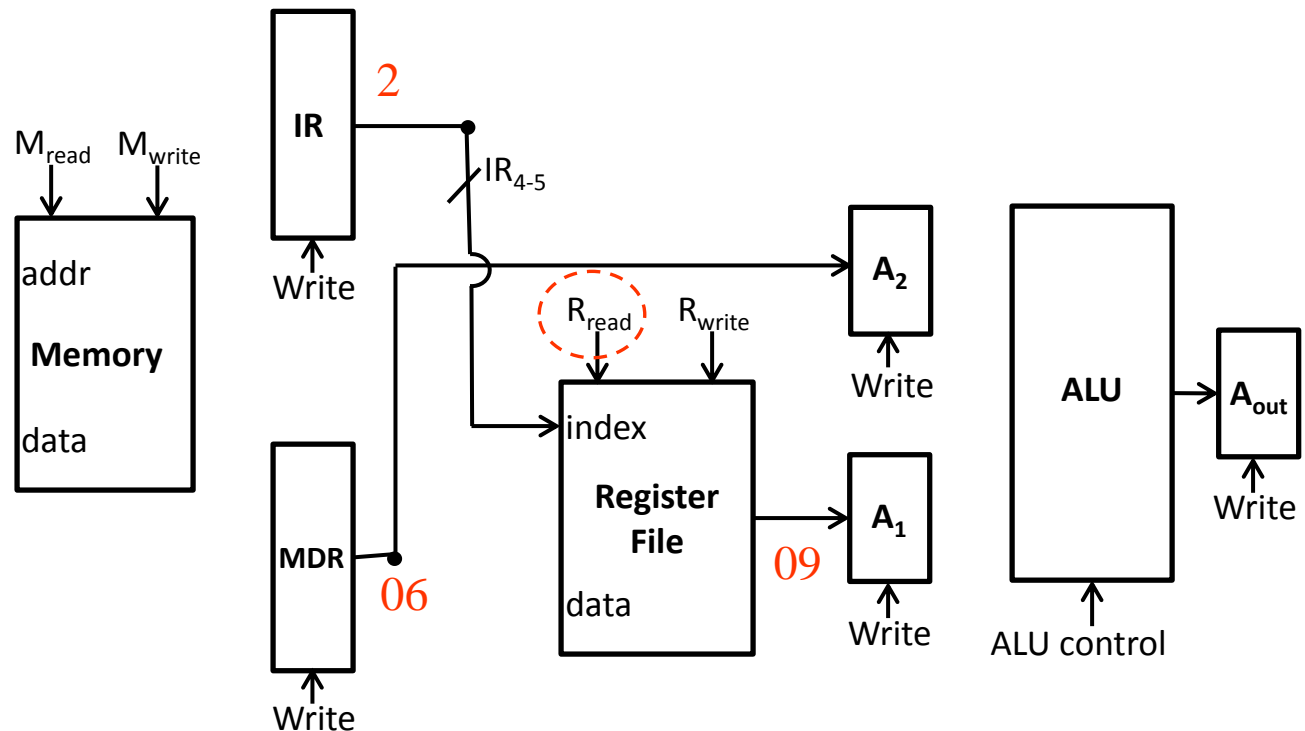ADD R2,[202]:
3. $A_1 = R[IR_{4..5}]$
 $A_2 = MDR$



if ALU Control = 0 then $A_{out} = A_1 + A_2$
 if ALU Control = 1 then $A_{out} = A_1 - A_2$

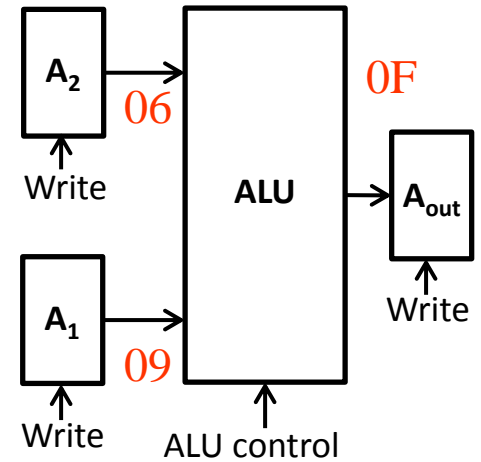  10 read/write signals
 1 ALU Control signal




ADD R2,[202]:
4. $A_{out} = A_1 + A_2$

if ALU Control = 0 then $A_{out} = A_1 + A_2$
 if ALU Control = 1 then $A_{out} = A_1 - A_2$




10 read/write signals
 1 ALU Control signal

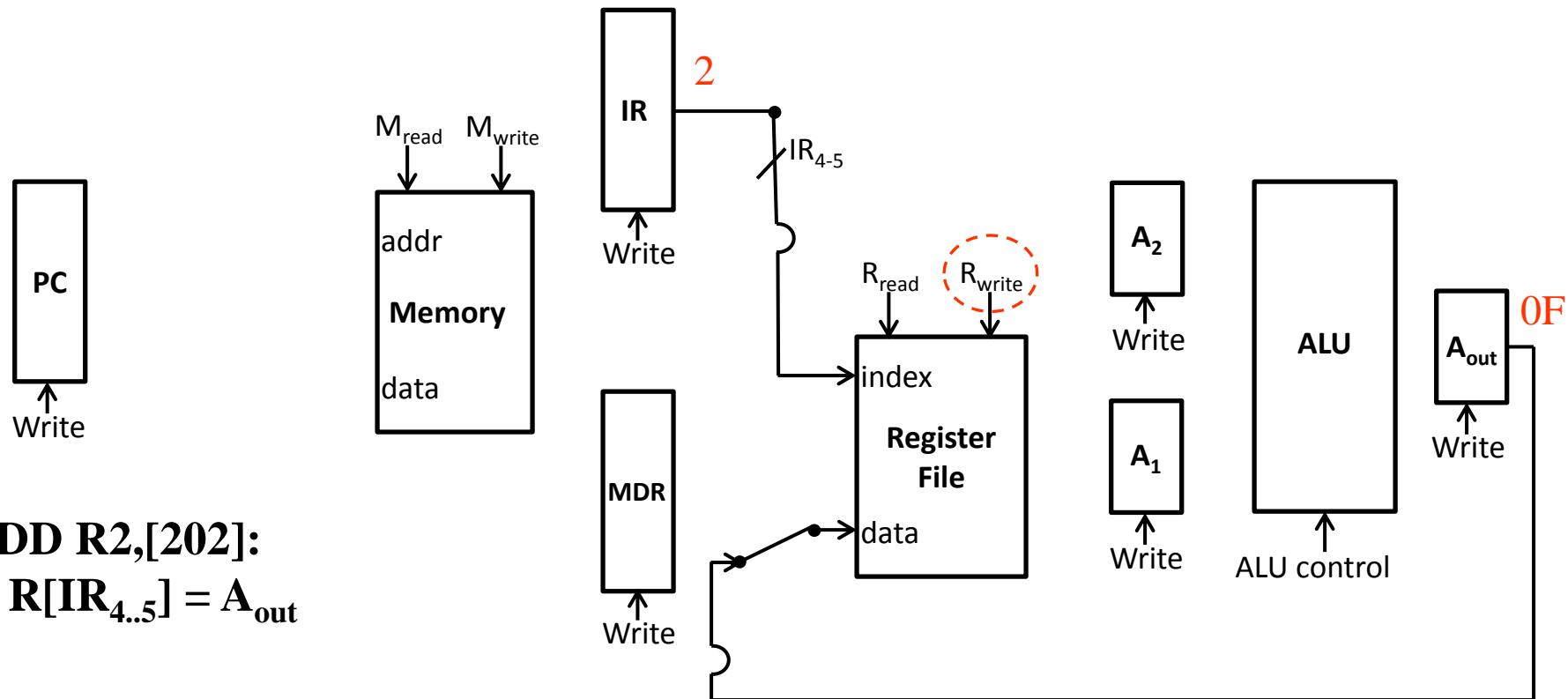ADD R2,[202]:
5. $R[IR_{4..5}] = A_{out}$



if ALU Control = 0 then $A_{out} = A_1 + A_2$
 if ALU Control = 1 then $A_{out} = A_1 - A_2$

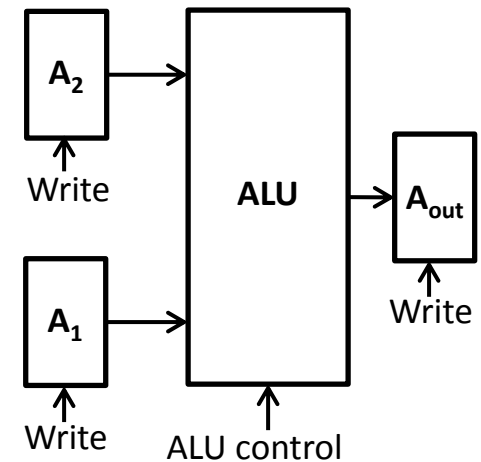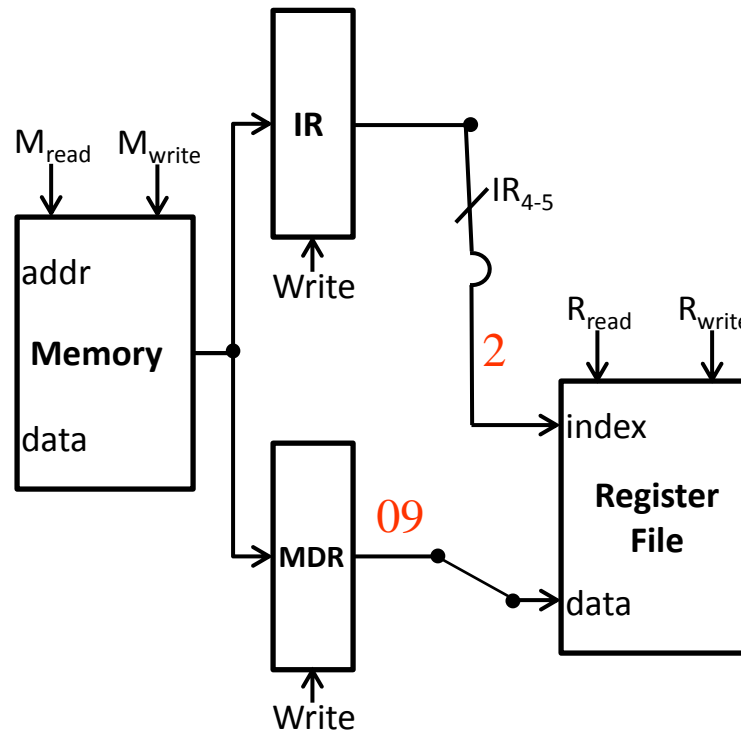 
10 read/write signals
 1 ALU Control signal



Recall:
LOAD R2,[201]:
3. $R[IR_{4..5}] = MDR$
and
ADD R2,[202]:
5. $R[IR_{4..5}] = A_{out}$

if ALU Control = 0 then $A_{out} = A_1 + A_2$
 if ALU Control = 1 then $A_{out} = A_1 - A_2$

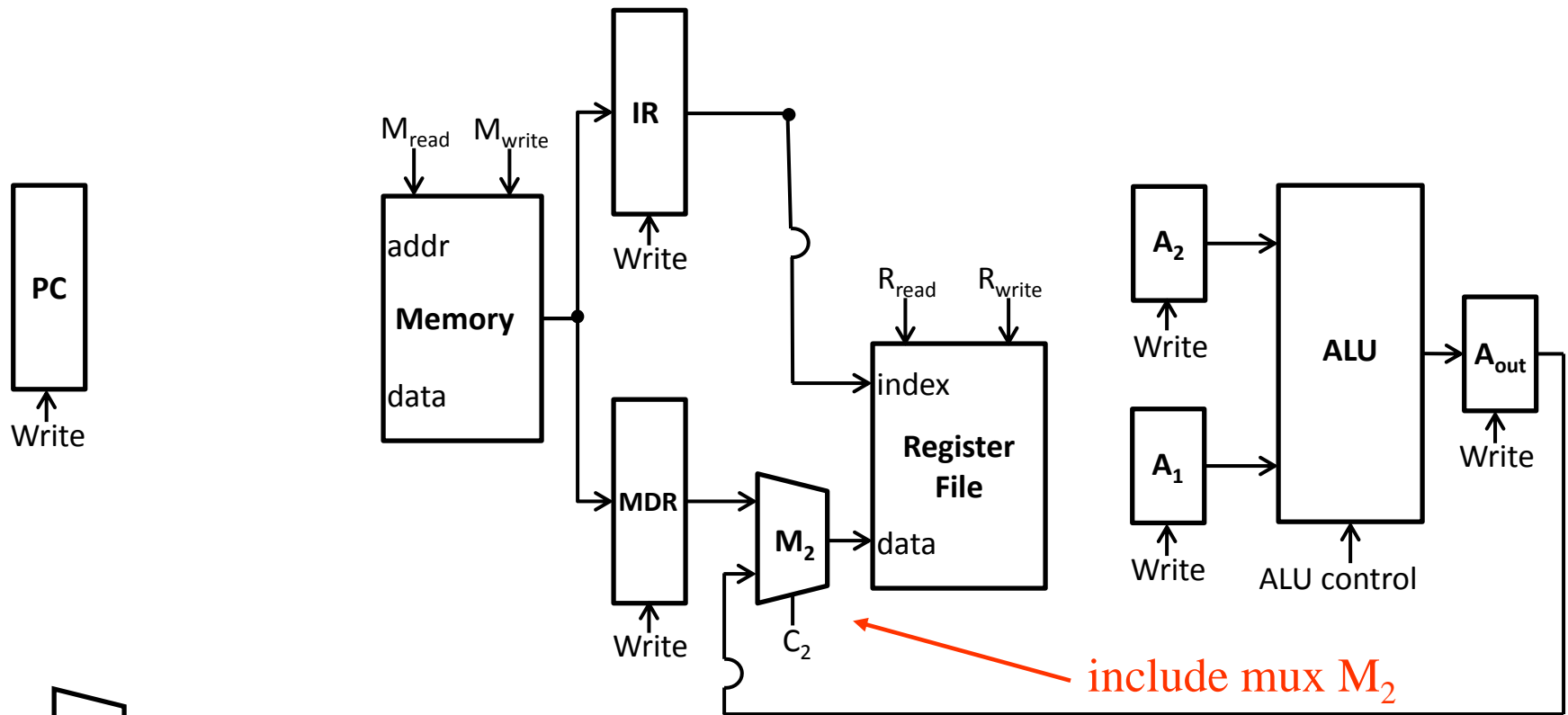
10 read/write signals
 1 ALU Control signal



include mux M_2


if ALU Control = 0 then $A_{out} = A_1 + A_2$
 if ALU Control = 1 then $A_{out} = A_1 - A_2$

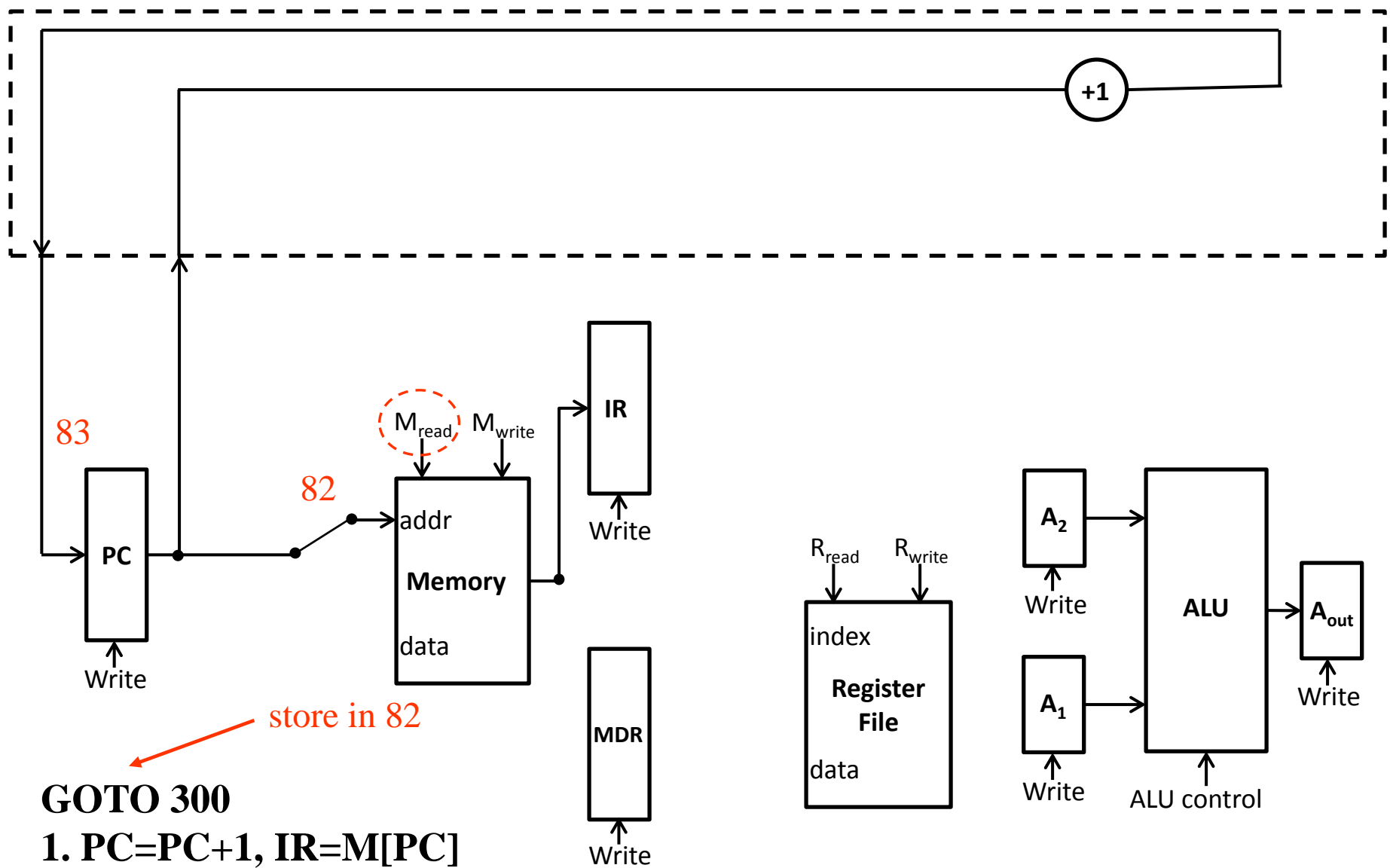10 read/write signals
 1 ALU Control signal
 1 multiplexer signal




if ALU Control = 0 then $A_{out} = A_1 + A_2$
 if ALU Control = 1 then $A_{out} = A_1 - A_2$

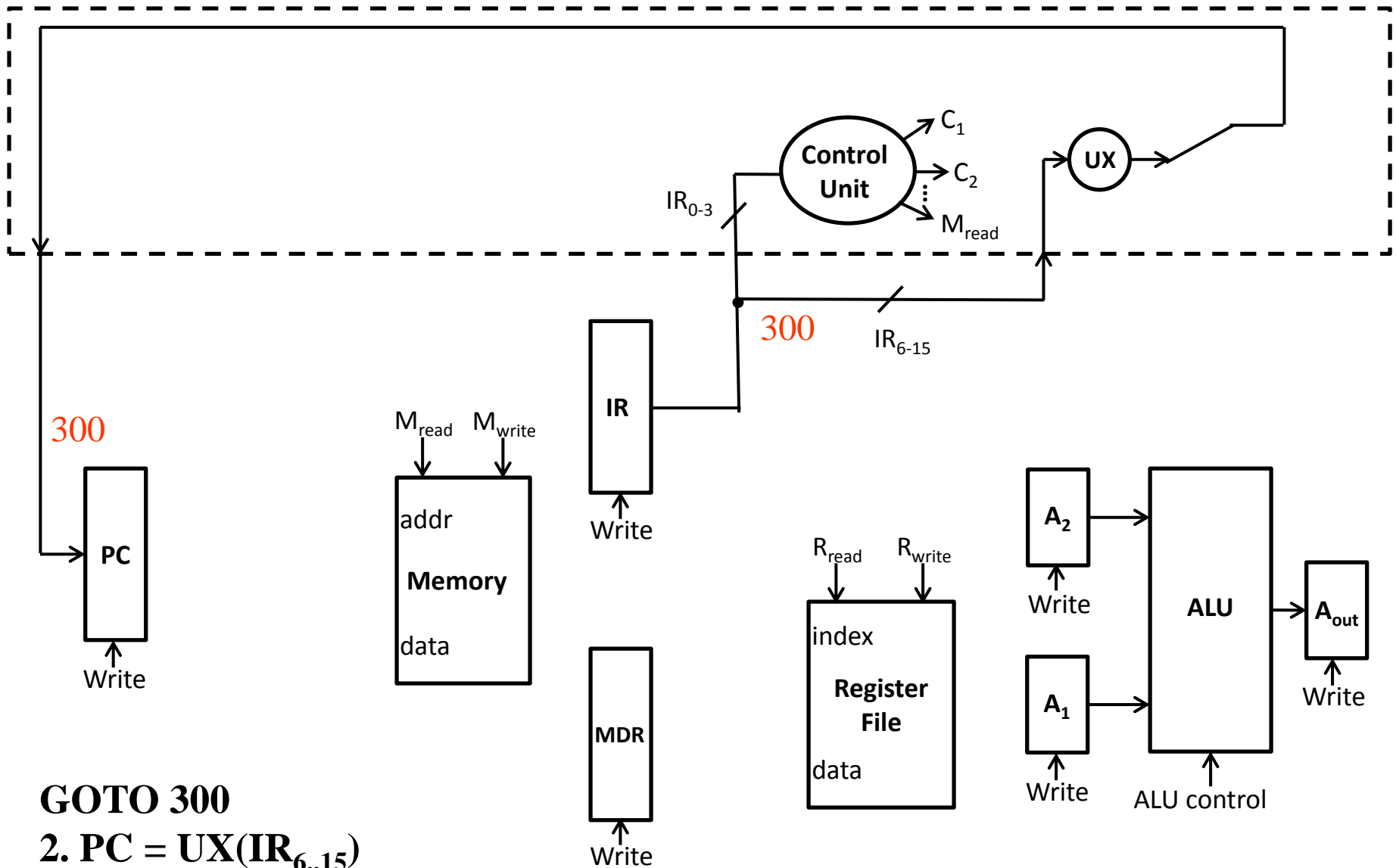10 read/write signals
 1 ALU Control signal




if ALU Control = 0 then $A_{out} = A_1 + A_2$
 if ALU Control = 1 then $A_{out} = A_1 - A_2$

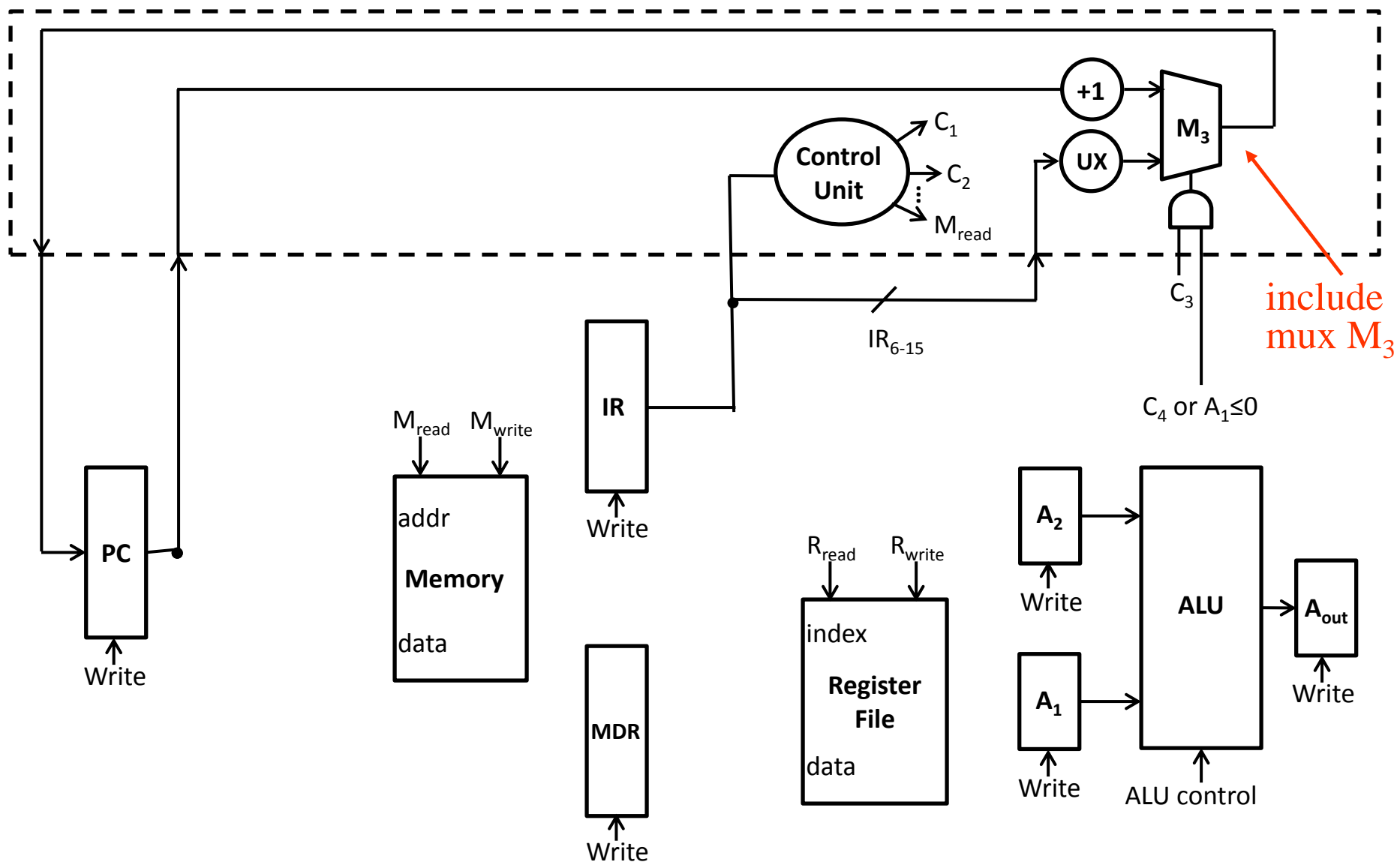10 read/write signals
 1 ALU Control signal



if ALU Control = 0 then $A_{out} = A_1 + A_2$
 if ALU Control = 1 then $A_{out} = A_1 - A_2$

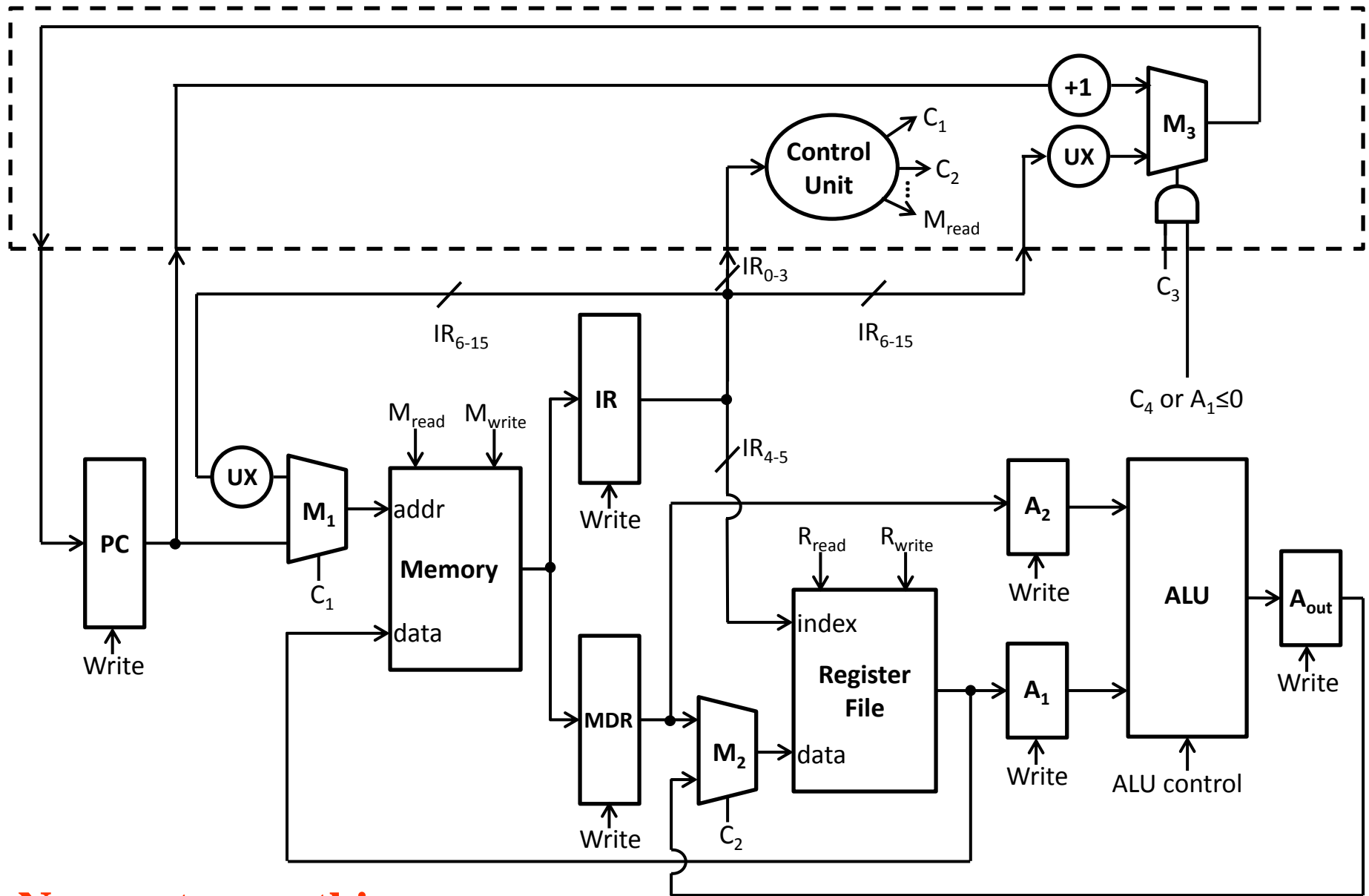10 read/write signals
 1 ALU Control signal
 2 multiplexer signals



Now put everything together!

if ALU Control = 0 then $A_{out} = A_1 + A_2$
 if ALU Control = 1 then $A_{out} = A_1 - A_2$

10 read/write signals
 1 ALU Control signal
 4 multiplexer signals